 


DSD_HW1_Report(b09901036 shi-lun chiu)

1.ALU

(1.) ALU_assign_tb : (screenshot of testing and nWave)

```
ash the programs that are using this file.
*Verdi* : Create FSDB file 'alu_assign.fsdb'
*Verdi* : Begin traversing the scopes, layer (0).
*Verdi* : End of traversing.
PASS --- 0100 boolean not
$finish called from file "alu_assign_tb.v", line 40.
$finish at simulation time 2500
VCS Simulation Report
Time: 25000 ps
CPU Time: 0.700 seconds; Data structure size: 0.0Mb
Tue Mar 28 14:59:45 2023
CPU time: .538 seconds to compile + .614 seconds to elab + .435 seconds to link + .7
45 seconds in simulation
```




(2.) ALU_assign_tb2 : (screenshot of testing and nWave)

```
alu_assign_test
0.ADD (signed)
[out = x + y]
.... passed.
1.SUB (signed)
[out = x + y]
.... passed.
2.BITAND
[out = and(x, y)]
.... passed.
3.BITOR
[out = OR(x, y)]
.... passed.
4.BITNOT
[out = ~x]
.... passed.
5.BITXOR
[out = xor(x,y)]
.... passed.
6.BITNOR
[out = nor(x , y)]
.... passed.
7.SLLV
[out = y << x[2:0]]
.... passed.
8.SLRV
[out = y >> x[2:0]]
.... passed.
9.SRA
```

```
.... passed.
8.SLRV
[out = y >> x[2:0]]
.... passed.
9.SRA
[out={x[7],x[7:1]}]
.... passed.
10.RL
[out = {x[6:0] , x[7]}]
.... passed.
11.RR
[out = {x[0] , x[7:1]}]
.... passed.
12.EQ
[out = (x = y)? 8'd1:8'd0]
.... passed.
12_2.EQ
[out = (x = y)? 8'd1:8'd0]
.... passed.
13.NOP
[out = 8'd0]
.... passed.
14.NOP
[out = 8'd0]
.... passed.
15.NOP
[out = 8'd0]
.... passed.
```

```
*****
**      Congratulations !!      **
** All Patterns Passed!!        **
*****
$finish called from file "alu_assign_tb2.v", line 224
```

```
/|_|/
/ 0,0 |
/ ^ ^ ^ \
| ^ ^ ^ |w|
\m m |
```

 

Ways of testing :

0.

```
err_count =0;
x          =8'b10010110;
y          =8'b00101101;
ctrl=4'd0;
```

1.

```
x          =8'b10110111;
y          =8'b00001101;
ctrl=4'd1;
```

2.

```
x          =8'b10110111;
y          =8'b11010101;
ctrl=4'd2;
```

3.

```
x          =8'b10110101;
y          =8'b10011101;
ctrl=4'd3;
```

4.

```
x          =8'b10111001;

ctrl=4'd4;
```

5.

```
x          =8'b10110111;
y          =8'b00101101;
ctrl=4'd5;
```

6.

```
x          =8'b10110101;
y          =8'b00100101;
ctrl=4'd6;
```

7.

```
x          =8'b01011010;
y          =8'b11001101;
ctrl=4'd7;
```

8.

```
x          =8'b01011011;
y          =8'b11001101;
ctrl=4'd8;
```

9.

```
ctrl=4'd9;
x          =8'b01001110;
y          =8'b11001101;
```

10.

```
x          =8'b10110101; //  
y          =8'b10100101;  
ctrl=4'd10;
```

11.

```
x          =8'b10110101; //  
y          =8'b10100101;  
ctrl=4'd11;
```

12.

```
x          =8'b10110101;  
y          =8'b10100101;  
ctrl=4'd12;
```

and

```
x          =8'b01101011;  
y          =8'b01101011;  
ctrl=4'd12;
```

13.

```
x          =8'b10110101;  
y          =8'b00100101;  
ctrl=4'd13;
```

14.

```
x          =8'b10110101;  
y          =8'b10100101;  
ctrl=4'd14;
```

15.

```
x          =8'b00110101;  
y          =8'b10101101;  
ctrl=4'd15;
```

(3.) ALU_always_tb : (screenshot of testing and nWave)

```
$finish called from file "alu_always_tb.v", line 40.  
$finish at simulation time 2500  
V C S   S i m u l a t i o n   R e p o r t  
Time: 25000 ps  
CPU Time: 0.740 seconds; Data structure size: 0.0Mb  
Tue Mar 28 15:11:06 2023  
CPU time: .547 seconds to compile + .435 seconds to elab + .575 seconds to link +  
84 seconds in simulation
```

(4.) ALU_always_tb2 : (screenshot of testing and nWave)

```

Verilog: End of traversing.

```

```


alu_assign_test
0.ADD (signed)
[out = x + y]
.... passed.
1.SUB (signed)
[out = x + y]
.... passed.
2.BITAND
[out = and(x, y)]
.... passed.
3.BITOR
[out = OR(x, y)]
.... passed.
4.BITNOT
[out = ~x]
.... passed.
5.BITXOR
[out = xor(x,y)]
.... passed.
6.BITNOR
[out = nor(x , y)]
.... passed.
7.SLLV
[out = y << x[2:0]]
.... passed.
8.SLRV
[out = y >> x[2:0]]
.... passed.
9.SRA
[out={x[7],x[7:1]]}
.... passed.
10.RL
[out = {x[6:0] , x[7]}]
.... passed.

```

```

8.SLRV
[out = y >> x[2:0]]
.... passed.
9.SRA
[out={x[7],x[7:1]]}
.... passed.
10.RL
[out = {x[6:0] , x[7]}]
.... passed.
11.RR
[out = {x[0] , x[7:1]}]
.... passed.
12.EQ
[out = (x == y)? 8'd1:8'd0]
.... passed.
12.2.EQ
[out = (x == y)? 8'd1:8'd0]
.... passed.
13.NOP
[out = 8'd0]
.... passed.
14.NOP
[out = 8'd0]
.... passed.
15.NOP
[out = 8'd0]
.... passed.
*****
**                               /|_|/
**                               / 0,0 |
** Congratulations !!          / ^ ^ ^ |
** All Patterns Passed!!       / ^ ^ ^ |w|
**                               \m m _|
*****
$finish called from file "alu_always_tb2.v", line 321.
$finish at simulation time 26500
VCS Simulation Report
Time: 265000 ps
CPU Time: 0.750 seconds; Data structure size: 0.0Mb
Tue Mar 20 22:53:56 2023
CPU time: .591 seconds to compile + .430 seconds to elab + .642 seconds to link + .801 seconds in simulation

```

 

Ways of testing : same as ALU_assign_tb,the

0.

```

err_count    =0;

x              =8'b10010110;
y              =8'b00101101;
ctrl=4'd0;

```

1.

```

x              =8'b10110111;
y              =8'b00001101;
ctrl=4'd1;

```

2.

```

x              =8'b10110111;
y              =8'b11010101;
ctrl=4'd2;

```

3.

```

x              =8'b10110101;
y              =8'b10011101;
ctrl=4'd3;

```

4.

```
x          =8'b10111001;
```

```
ctrl=4'd4;
```

5.

```
x          =8'b10110111;  
y          =8'b00101101;  
ctrl=4'd5;
```

6.

```
x          =8'b10110101;  
y          =8'b00100101;  
ctrl=4'd6;
```

7.

```
x          =8'b01011010;  
y          =8'b11001101;  
ctrl=4'd7;
```

8.

```
x          =8'b01011011;  
y          =8'b11001101;  
ctrl=4'd8;
```

9.

```
ctrl=4'd9;  
x          =8'b01001110;  
y          =8'b11001101;
```

10.

```
x          =8'b10110101; //  
y          =8'b10100101;  
ctrl=4'd10;
```

11.

```
x          =8'b10110101; //  
y          =8'b10100101;  
ctrl=4'd11;
```

12.

```
x          =8'b10110101;  
y          =8'b10100101;  
ctrl=4'd12;
```

and

```
x          =8'b01101011;  
y          =8'b01101011;  
ctrl=4'd12;
```

13.

```
x          =8'b10110101;
```

```

y          =8'b00100101;
ctrl=4'd13;

```

14.

```

x          =8'b10110101;
y          =8'b10100101;
ctrl=4'd14;

```

15.

```

x          =8'b00110101;
y          =8'b10101101;
ctrl=4'd15;

```


2. 8 X 8 register file

(1.) screenshot of testing and nWave

```

8 X 8 bits register file test
1: store A=107 in REG#1
.... passed.
2: store B=227 in REG#5
.... passed.
3: store C=227 in REG#2
.... passed.
4: store D=181 in REG#4 and look back C=146 in REG#2
.... passed.
5: restore multiplicand E=116 in REG#1
.... passed.
6: test #reg0
.... passed.
*****
**                               **      /|_ |
**                               **      / 0,0 |
** Congratulations !!          **      /_____|
** All Patterns Passed!!        **      / ^ ^ ^ \ |
**                               **      | ^ ^ ^ ^ |w|
**                               **      \m__m__|_|
*****
$finish called from file "register_file_tb.v", line 175.
$finish at simulation time          13000
VCS Simulation Report
Time: 130000 ps
CPU Time:      0.720 seconds;      Data structure size:  0.0Mb

```

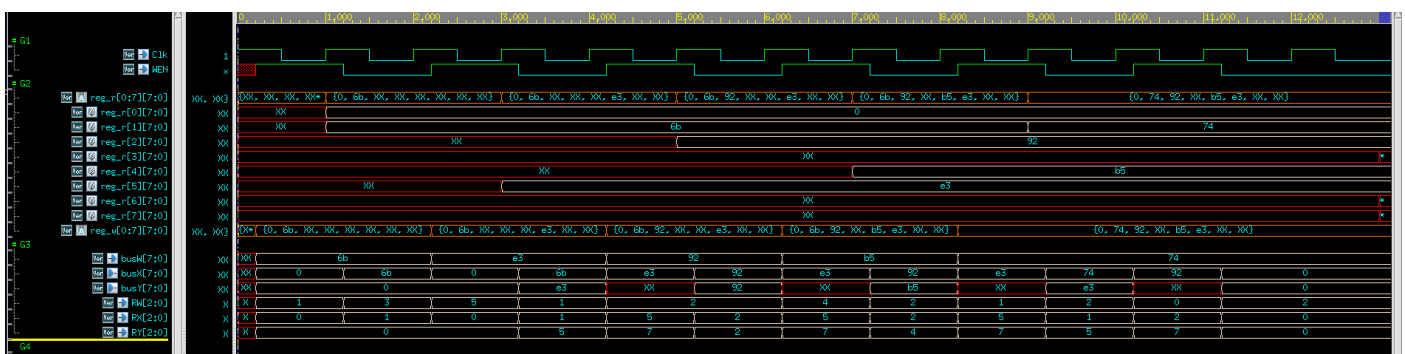

```

module register_file_tb;

    // port declaration for design-under-test
    reg Clk, WEN;
    reg [2:0] RW, RX, RY;
    reg [7:0] busW;
    wire [7:0] busX, busY;

    // instantiate the design-under-test
    register_file rf(
        Clk ,
        WEN ,
        RW ,
        busW ,
        RX ,
        RY ,
        busX ,
        busY
    );

    // write your test pattern here
    initial begin
        $fsdbDumpfile("register_file.fsdb");
        $fsdbDumpvars (0, register_file_tb , "+mda");

    end

    // clock generation
    always#(`HCYCLE) Clk = ~Clk;

    //test pattern
    parameter A ={4'd6,4'd11};
    parameter B ={4'd14,4'd3};
    parameter C ={4'd9,4'd2};
    parameter D ={4'd11,4'd5};
    parameter E ={4'd7,4'd4};

    //simulation count
    integer err_count;
    initial begin

        Clk          = 1'b1;
        err_count = 0;

```

```

$display( " 8 X 8 bits register file test" );

//-----2 cycle testbench-----
#(`CYCLE*0.2)
$display( "1: store  A=%3d in REG#1 " , A );
WEN = 1'b1 ; RW = 3'd1 ; busW = A ; RX = 3'd0 ;
RY = 3'd0 ;
#(`CYCLE*0.8)
#(`CYCLE*0.2)
WEN = 1'b0 ; RW = 3'd3 ; RX = 3'd1 ; RY = 3'd0 ;
#(`CYCLE*0.3)
if( busX==A ) $display( "      .... passed." );
else begin
    err_count = err_count+1;
    $display( "      .... failed, design(%b) != expected(%b)", busX, A );
end
#(`HCYCLE)

//-----2 cycle testbench-----
#(`CYCLE*0.2)
$display( "2: store  B=%3d in REG#5 " , B );
WEN = 1'b1 ; RW = 3'd5 ; busW = B ; RX = 3'd0 ;
RY = 3'd0 ;
#(`CYCLE*0.8)
#(`CYCLE*0.2)
WEN = 1'b0 ; RW = 3'd1 ; RX = 3'd1 ; RY = 3'd5 ;
#(`CYCLE*0.3)
if( busY==B ) $display( "      .... passed." );
else begin
    err_count = err_count+1;
    $display( "      .... failed, design(%b) != expected(%b)", busX, A );
end
#(`HCYCLE)

//-----2 cycle testbench-----
#(`CYCLE*0.2)
$display( "3: store  C=%3d in REG#2 " , B );
WEN = 1'b1 ; RW = 3'd2 ; busW = C ; RX = 3'd5 ;
RY = 3'd7 ;
#(`CYCLE*0.8)
#(`CYCLE*0.2)
WEN = 1'b0 ; RW = 3'd2 ; RX = 3'd2 ; RY = 3'd2 ;

```



```

#(`CYCLE*0.3)
if( busY==C & busX == C ) $display( "    .... passed." );
else begin
    err_count = err_count+1;
    $display( "    .... failed, designX(%b) != expected(%b)", busX, C );
    $display( "    .... failed, designY(%b) != expected(%b)", busY, C );
end
#(`HCYCLE)

//-----2 cycle testbench-----
#(`CYCLE*0.2)
$display( "4: store D=%3d in REG#4 and look back C=%3d in REG#2" , D ,C);
WEN = 1'b1 ; RW = 3'd4 ; busW = D ; RX = 3'd5 ;
RY = 3'd7 ;
#(`CYCLE*0.8)
#(`CYCLE*0.2)
WEN = 1'b0 ; RW = 3'd2 ; RX = 3'd2 ; RY = 3'd4 ;
#(`CYCLE*0.3)
if( busY == D && busX ==C ) $display( "    .... passed." );
else begin
    err_count = err_count+1;
    $display( "    .... failed, designX(%b) != expected(%b)", busX, C );
    $display( "    .... failed, designY(%b) != expected(%b)", busY, D );
end
#(`HCYCLE)

//-----2 cycle testbench-----
#(`CYCLE*0.2)
$display( "5: restore multiplicand E=%3d in REG#1 " , E );
WEN = 1'b1 ; RW = 3'd1 ; busW = E ; RX = 3'd5 ;
RY = 3'd7 ;
#(`CYCLE*0.8)
#(`CYCLE*0.2)
WEN = 1'b0 ; RW = 3'd2 ; RX = 3'd1 ; RY = 3'd5 ;
#(`CYCLE*0.3)
if( busX == E ) $display( "    .... passed." );
else begin
    err_count = err_count+1;
    $display( "    .... failed, design(%b) != expected(%b)", busX, E);
end
#(`HCYCLE)

```

```

//-----2 cycle testbench-----
#(`CYCLE*0.2)
$display( "6: test #reg0 " );
WEN = 1'b1 ; RW = 3'd0 ; busW = E ; RX = 3'd2 ;
RY = 3'd7 ;
#(`CYCLE*0.8)
#(`CYCLE*0.2)
WEN = 1'b0 ; RW = 3'd2 ; RX = 3'd0 ; RY = 3'd0 ;
#(`CYCLE*0.3)
if( busX == 8'd0 ) $display( " .... passed." );
else begin
    err_count = err_count+1;
    $display( " .... failed, design(%b) != expected(%b)", busX,8'd0 );
end
#(`HCYCLE)

if( err_count==0 ) begin
$display("***** /|_|/");
$display("**          ** / 0,0 |");
$display("** Congratulations !! ** /____ |");
$display("** All Patterns Passed!! ** / ^ ^ ^ \ \ |");
$display("**          ** | ^ ^ ^ ^ |w|");
$display("***** \ \ m__m__|_|");
end
else begin
$display("***** ");
$display(" Failed ,and ... ");
$display("..... /´ /");
$display("..... ..,./´ ..//");
$display("..... ..,/´ ..//");
$display("..... ./... ..//");
$display("...../´´/´ ...´/´´•.");
$display("...../´/.../... ./... ..../´´|.");
$display(".....(´(...´(... .....,~/´...´)");
$display(".....|..... ..../.../");
$display(".....|..... ..../...´´.´");
$display(".....|..... ..../...´´.");
$display(".....|..... ..../...´´.");
$display(" Total %2d Errors ... ", err_count );
$display("***** ");

```

```
end
    #(`CYCLE) $finish;
end
endmodule
```

3. simple Caculator

(1)

```

6: set REG#6 = (B[3]==1)? 8'b11111111: 8'b00000000
   [REG#2 = sra REG#2]
   [REG#6 = and 0000_0001 REG#2]
   [REG#6 = sub REG#0 REG#6]
   .... passed.

7: shift & summation, REG#7 = A*B[0]
   [REG#3 = and REG#1 REG#3]
   [REG#7 = add REG#0 REG#3]
   .... passed.


8: shift & summation, REG#7 = A*B[1:0]
   [REG#4 = and REG#1 REG#4]
   [REG#4 = sll 0000_0001 REG#4]
   [REG#7 = add REG#7 REG#4]
   .... passed.

9: shift & summation, REG#7 = A*B[2:0]
   [REG#5 = and REG#1 REG#5]
   [REG#5 = sll 0000_0010 REG#5]
   [REG#7 = add REG#7 REG#5]
   .... passed.

          300
10: shift & summation, REG#7 = A*B
   [REG#6 = and REG#1 REG#6]
   [REG#6 = sll 0000_0011 REG#6]
   [REG#7 = add REG#7 REG#6]
   .... passed.

Calculation results: 13 * 12 = 156
*****
**                                     /|_|/|
**                                     / 0,0 |
**   Congratulations !!             /_____|
**   All Patterns Passed!!          / ^ ^ ^ \ |
**                                     | ^ ^ ^ ^ |w|
*****                               \m   m |

```

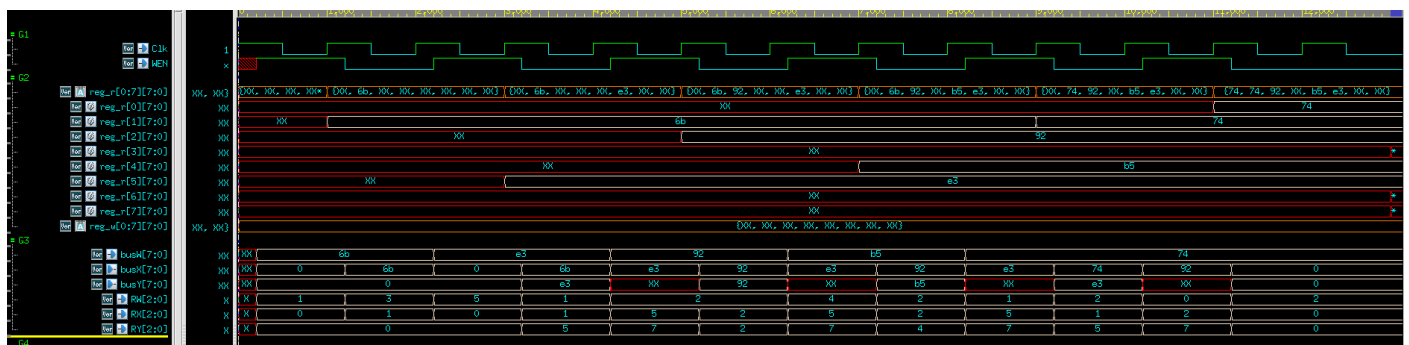

(2) use it given testbench

what I found

In ALU I know that case can be only use in always block ,and assign can only be used by wire announcement .

In register file I knew that in sequential circuit can use clock gating to prevent unwanted result

The last simple calculator is relatively simple if ALU and register files are finished.